

Thur.

Basic Questions about a laser (= negative conductance oscillator)

1. What are 3 essential elements to construct a laser?

- {① frequency selective element : LC circuit, delayed feedback loop, Fabry-Perot, ring, distributed
- ② amplifying element (negative conductance device) : tunnel diode, IMPATT diode, Gunn diode, Josephson junction, pn junction
- ③ nonlinear element (amplitude limiting device) : gain saturation

2. What is the electrical circuit element that represents a gain?

negative conductance
differential.

3. What is the mechanism for spectral purification in a laser?

below threshold : frequency selective amplification/deamplification

above threshold : phase coherent stimulated emission of photons

4. What is the mechanism for amplitude stabilization in a laser?

gain saturation (relaxation oscillation)


5. What is the energy source (seed) for laser oscillation?

noise

6. What is the single most important parameter that determines the dynamics of a laser?

spontaneous emission coupling efficiency = saturation parameter



Thur.

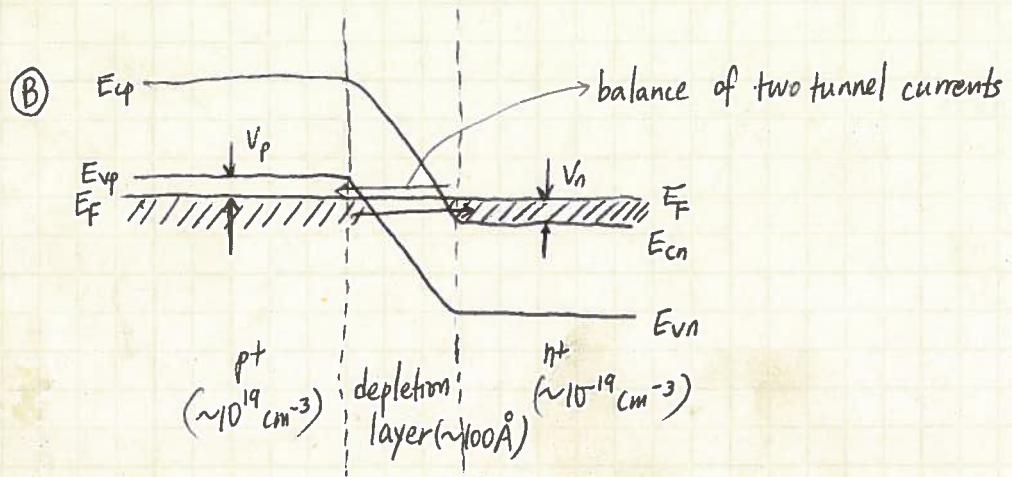pn Tunnel Junction (Esaki diode)current noise


$$S_I(w) = 2g I \coth\left(\frac{qV}{2k_B\Theta}\right)$$

$$V \approx 0 \rightarrow S_I(w) = \frac{4k_B\Theta}{q}$$


$$V > V_T \rightarrow S_I(w) = 2g I$$

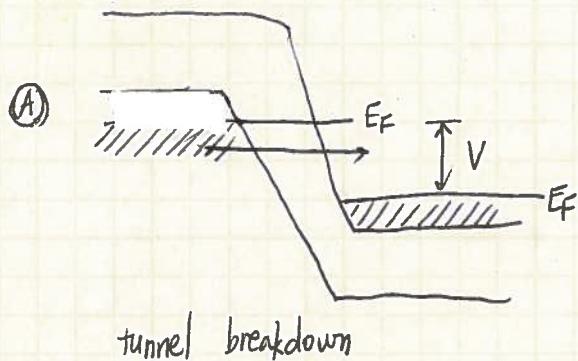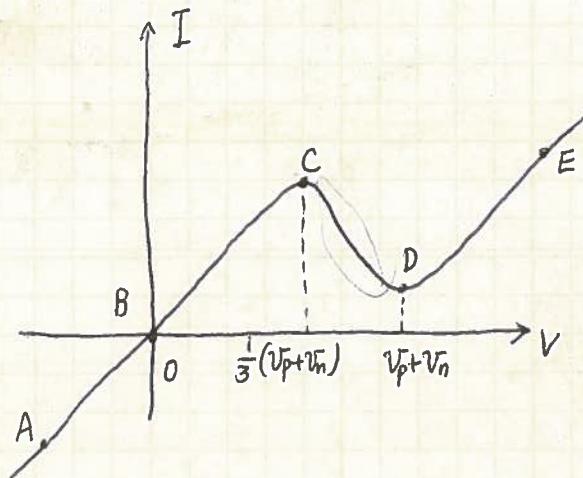


tunnel breakdown

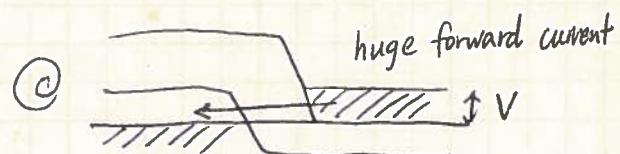

peak tunnel current

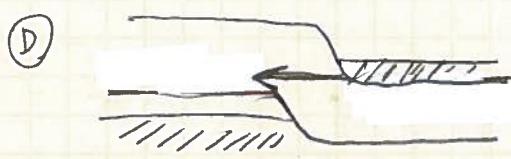



no tunnel current

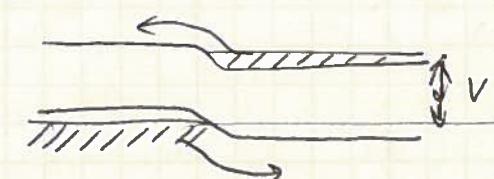

thermal diffusion current

Thur.

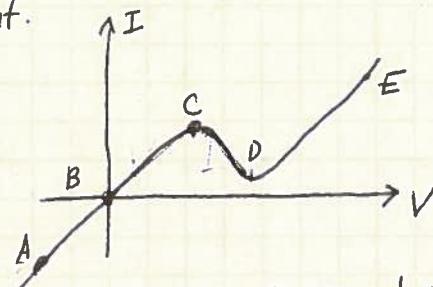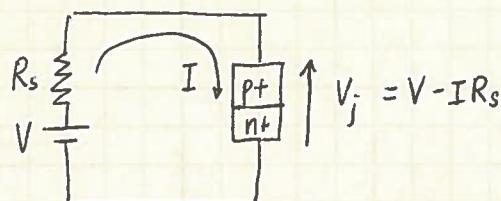Amplification by a Negative Conductance Element.



If a p⁺-n⁺ junction diode is biased at V > 0 between the points B and C,

the differential conductance $\frac{dI}{dV}$ is "positive"

increased current $I \uparrow \rightarrow V_j \downarrow \rightarrow I \downarrow$ decreased current

decreased current $I \downarrow \rightarrow V_j \uparrow \rightarrow I \uparrow$ increased current

this negative feedback mechanism attenuates a current fluctuation

\therefore sys is stable, small fluctuation ✓

If a p⁺-n⁺ junction diode is biased at V > 0 btw C & D,

the differential conductance $\frac{dI}{dV}$ is "negative".

increased current $I \uparrow \rightarrow V_j \downarrow \rightarrow I \uparrow \uparrow \rightarrow V_j \downarrow \downarrow \rightarrow I \uparrow \uparrow \uparrow \rightarrow$

decreased current $I \downarrow \rightarrow V_j \uparrow \rightarrow I \downarrow \downarrow \rightarrow V_j \uparrow \uparrow \rightarrow I \downarrow \downarrow \downarrow \rightarrow$

This positive feedback mechanism amplifies a current fluctuation




A negative conductance element such as a tunnel diode features a gain and is used as an amplifier and an oscillator.

Thur.

Negative Conductance (van der Pol) oscillators


physical process of "self-oscillation"

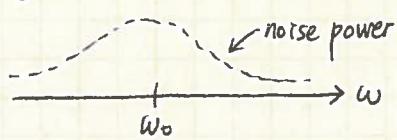- An amplifying element generates a broad band noise.




When gain is max,
noise power is max.

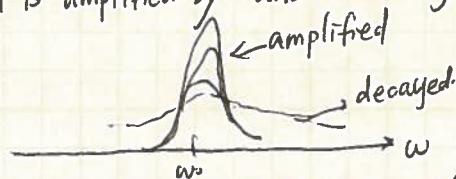
- A frequency selective circuit stores a specific frequency component that is amplified by unsaturated gain



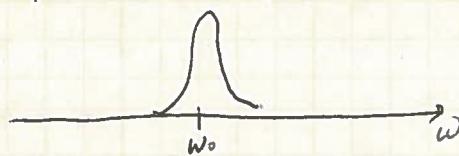- A nonlinear element stops this amplification process "spontaneous" amplification via "self-feedback" regeneration




→ stabilized amplitude,
narrow band signal.

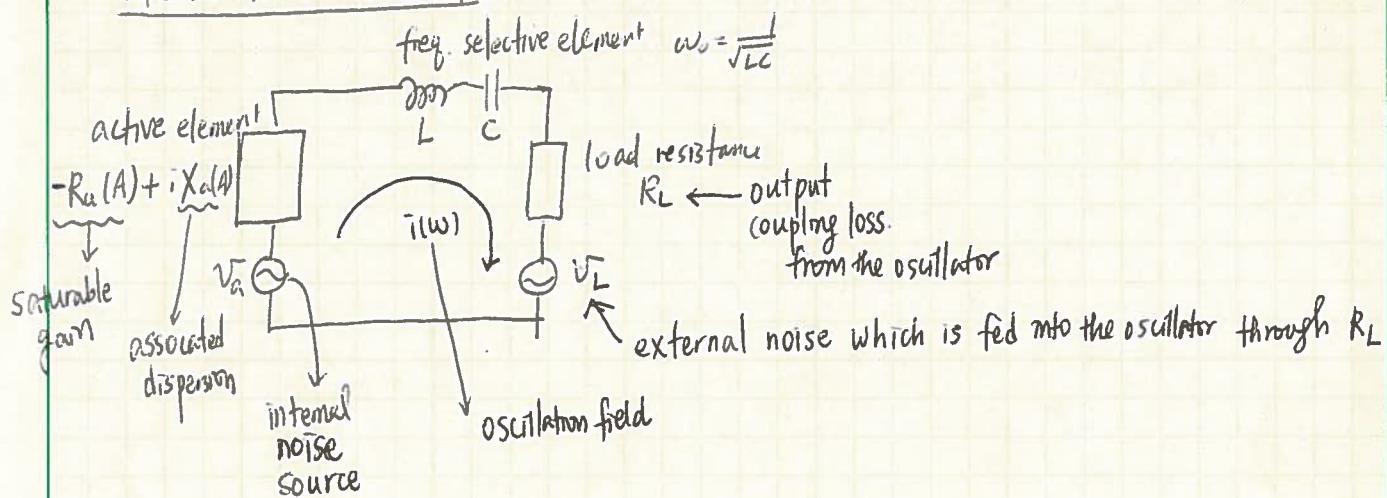Electrical circuit modelVan der Pol oscillator

the first person to study the noise properties of a negative conductance oscillator

Phil. Mag. Series 7, 3, 65 (1927)

Thur

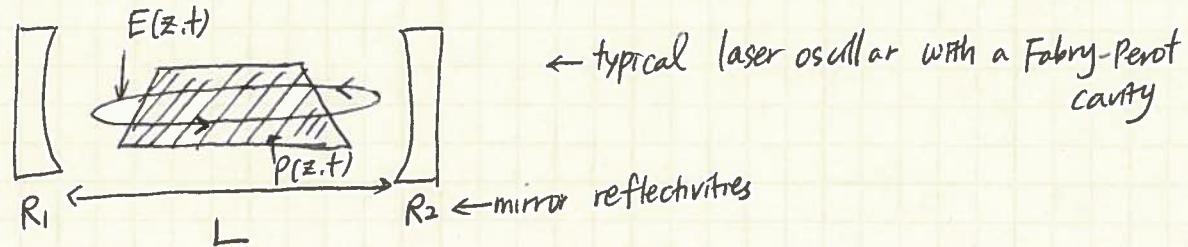

$$\text{photon decay rate } \frac{\omega}{Q} = \frac{c}{2L} \ln \frac{1}{R_1 R_2} \quad Q = \text{cavity-Q-value}$$

$L = \text{cavity length.}$

an oscillation field : electric field

$$E(z,t) = \frac{1}{2} \sum_n E_n(t) e^{i(w_n t + \phi_n)} \quad \begin{matrix} \uparrow \text{amplitude} \\ \uparrow \text{phase} \end{matrix} \quad U_n(z) + \text{C.C.}$$

an inverted medium : atomic polarization ensemble

$$P(z,t) = \frac{1}{2} \sum_n P_n(t) e^{i(w_n t + \phi_n)} \quad \begin{matrix} \uparrow \text{(U}_n(z)\text{)} \\ \uparrow \text{n = a longitudinal mode} \end{matrix} \quad \begin{matrix} \rightarrow \text{a spatial mode fn.} \\ \text{+ C.C.} \end{matrix}$$

Assume a single transverse mode operation.

Maxwell equation with a driving term.

$$\rightarrow -\frac{\partial^2 E}{\partial z^2} + \mu_0 \sigma \frac{\partial E}{\partial t} + \mu_0 \epsilon_0 \frac{\partial^2 E}{\partial t^2} = -\mu_0 \frac{\partial^2 P}{\partial t^2} \quad \begin{matrix} \leftarrow \text{driving term} \\ \text{by inverted atoms} \end{matrix}$$

↑ damping due to internal loss

equations of motion for the amplitude and phase of the oscillation field.

$$\dot{E}_n = -\frac{1}{2} \left(\frac{w_n}{Q} \right) E_n - \frac{1}{2} \left(\frac{w_n}{\epsilon_0} \right) \text{Im}(P_n) \quad \begin{matrix} \leftarrow \text{gain/loss:} \\ \text{- quadrature phase of } P_n \end{matrix}$$

$$\dot{\phi}_n = (\Omega_n - w_n) - \frac{1}{2} \left(\frac{w_n}{\epsilon_0} \right) \frac{1}{E_n} \text{Re}(P_n) \quad \begin{matrix} \leftarrow \text{dispersion} \\ \text{in-phase of } P_n \end{matrix}$$

$$\frac{w_n}{Q} = \frac{\sigma}{\epsilon_0} \quad \text{photon decay rate}$$

Ω_n = empty cavity resonant freq.

w_n = actual oscillation freq.

Complex susceptibility
 $P_n = \epsilon_0 \chi_m E_n$
 $= \epsilon_0 (\chi_{nr} + i \chi_{ni}) E_n$

$$\Rightarrow \quad \begin{aligned} \dot{E}_n &= -\frac{1}{2} \frac{w_n}{Q} E_n - \frac{1}{2} w_n \chi_{ri} E_n \\ \dot{\phi}_n &= (\Omega_n - w_n) - \frac{1}{2} w_n \chi_{nr} \end{aligned}$$


} laser Master eq.

Thur

Steady-state solutions of the laser master eq.

$$\frac{\omega_n}{Q} = \omega_n \chi_{ni} \quad \leftarrow \text{gain} = \text{loss}, \text{ threshold condition}$$
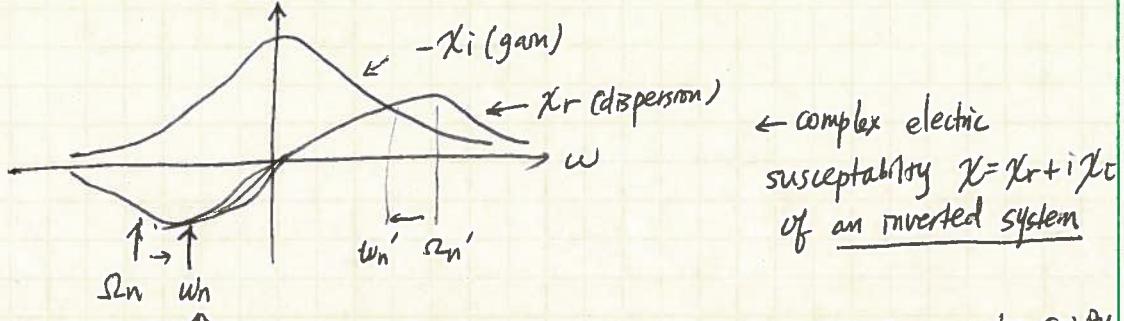
$$\omega_n = \Omega_n - \frac{1}{2} \omega_n \chi_{nr} \quad \leftarrow \text{oscillation freq.}$$



\leftarrow complex electric susceptibility $\chi = \chi_r + i\chi_i$
of an inverted system

ω_n is always pulled toward the gain center from the empty cavity freq. Ω_n due to the dispersion.

If the cavity internal electric field amplitude is normalized to represent a "photon amplitude", the stored energy is given by

$$E = \hbar \omega A_0^2 = \frac{1}{2} L A^2 \rightarrow \text{the eq. oscillation current amplitude in the LC circuit}$$

↑
photon field amplitude. $A_0^2 = n$, photon # $\text{e.g. } \mathbf{I}(\omega) = A_0 \cos \omega t$

$$\therefore A_0 = \sqrt{\frac{L}{2\hbar\omega}} A \quad \text{relation btw the photon field amplitude } A_0 \text{ & the eq. current amplitude } A$$

\therefore The output optical power from the laser,

$$P_{out} = \hbar \omega A_0^2 \underbrace{\left(\frac{w}{Q_{ex}} \right)}_{\text{photon decay rate}} = \frac{1}{2} R_L A^2$$

$$\text{photon decay rate} = \frac{R_L}{L}$$

The internally generated power

$$P_m = \hbar \omega A_0^2 \underbrace{\omega \chi_i(A_0)}_{\text{photon amplification rate}} = \frac{1}{2} R_a A^2$$

$$\text{photon amplification rate} = \frac{R_a(A)}{L}$$

The actual oscillation freq.

$$\omega = \Omega - \underbrace{\frac{1}{2} \omega \chi_r(A_0)}_{\text{dispersion}} = \Omega - \frac{1}{2L} X_a(A)$$

$$\text{dispersion} = \frac{X_a(A)}{L}$$

1:1 correspondence table

electrical circuit	Q Electro
oscillation field amp	$\sqrt{\frac{L}{2}} A$
photon decay rate	$\frac{R_L}{L}$
photon amplification rate	$\frac{R_a(A)}{L}$
Dispersion	<u>$X_a(A)$</u>
	$w \chi_r(A)$

Thur

$$\omega L - \frac{1}{\omega C} = \frac{L}{\omega} \left(\omega^2 - \frac{1}{LC} \right) = \frac{L}{\omega} (\omega + \omega_0)(\omega - \omega_0) \approx 2L(\omega - \omega_0)$$

if ω is close to ω_0 .

\therefore circuit eq. becomes

$$\operatorname{Re} \left\{ [R_L - R_a(A) - \frac{\partial R_a}{\partial A} \Delta A + i 2L(\omega - \omega_0) + i \left(X_a(A) + \frac{\partial X_a}{\partial A} \Delta A \right)] (A + \Delta A) e^{i(\omega t + \Delta \phi)} \right\}$$

$$= V_a(t) + V_L(t).$$


replacing $i\Omega = i(\omega - \omega_0)$ by $\frac{d}{dt}$, & taking the time derivative

$$\operatorname{Re} \left\{ [R_L - R_a(A) - i 2L \left(\omega - \omega_0 + \frac{X_a(t)}{2L} \right) + 2L \left(\frac{1}{A} \frac{d \Delta A}{dt} - \frac{1}{2L} \frac{\partial R_a}{\partial A} \Delta A \right) + i 2L \left(\frac{d \Delta \phi}{dt} + \frac{1}{2L} \frac{\partial X_a}{\partial A} \Delta A \right)] A e^{i(\omega t + \Delta \phi)} \right\} = V_a(t) + V_L(t)$$

Suppose $\Delta A(t) = \Delta \phi(t) = V_a(t) = V_L(t) = 0$,

steady-state solutions: $R_L = R_a(A) = \frac{R_o}{1 + \beta A^2}$, $\omega = \omega_0 - \frac{X_a(A)}{2L}$

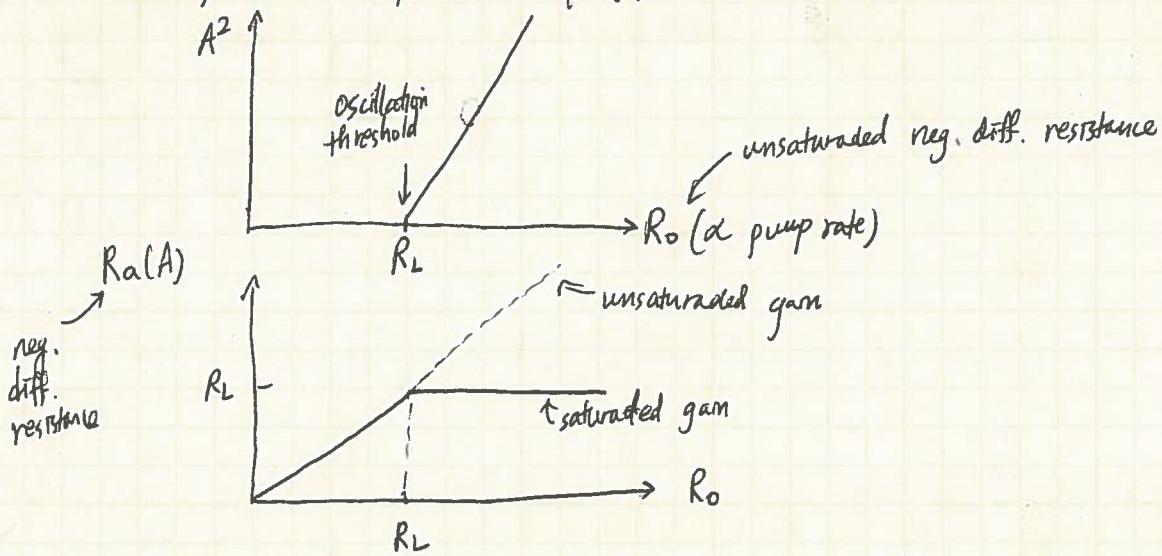steady-state oscill. amplitude $A^2 = \frac{1}{\beta} \left(\frac{R_o}{R_L} - 1 \right)$



relaxation oscillation process

① when oscillation field increases above the s.s. value ($A^2 = \frac{1}{\beta} \left(\frac{R_o}{R_L} - 1 \right)$)

the saturated gain decreases to below $R_L \Rightarrow$ the circuit has a net loss.

oscillation field \downarrow

② when oscillation field decrease below the ss. value,

the saturated gain increases above $R_L \Rightarrow \exists$ a net gain \therefore oscillation field amplified.

stabilize both the oscillation field amplitude & the saturated gain.

Thur.

Free-Running Van der Pol Oscillators

regenerative amplification

active element pumped by an external energy source
 ↓
 a negative diff. conductance (gain) realized
 ↓
 internal external noise voltages amplified
 ↓

the fluctuation freq. component of $i(w)$ grows near $\omega = \frac{1}{\sqrt{LC}}$

Once $R_a = R_L$, the active element negative resistance balances the positive load resistance,
 the circuit becomes unstable & spectral shape is purified.
 the noise grows exponential

∴ circuit oscillates & the steady-state coherent field amp. is established
 the steady-state condition is established by the gain-saturation of the active element

then broad band noise V_a, V_L are transformed into

a coherent wave with stabilized amplitude
 & a well-defined freq.

- ✓ frequency-selective amplification purifies spectral profile
- ✓ gain saturation stabilized the amplitude

circuit eq. of $i(w)$

$$\left[R_L + i \left(wL - \frac{1}{wC} \right) - R_a + iX_a \right] i(w) = V_a(w) + V_L(w)$$

Suppose $i(t) \equiv \operatorname{Re}(i(w)) = \operatorname{Re} [(A + \Delta A) e^{i(wt + \Delta \phi)}]$

$$= (A + \Delta A(t)) \cos(\omega t + \Delta \phi(t))$$

↑ average amplitude
 slowly varying amplitude & phase fluctuations

gain saturation of the active element

$$-R_a = \frac{-R_0}{1 + \beta A^2} \quad \begin{aligned} -R_0 &= \text{unsaturated negative differential resistance} \\ &\rightarrow \propto \text{Pump rate} \end{aligned}$$

if $|\Delta A| \ll 1$, linearize R_a & X_a : $R_a = R_a(A) + \frac{\partial R_a}{\partial A} \Delta A$

$$X_a = X_a(A) + \frac{\partial X_a}{\partial A} \Delta A$$

Amplitude and Phase Noise of an Internal Field

The small fluctuating parts

$$\begin{aligned} \left(2L\frac{d}{dt}\Delta A - A\frac{\partial R_a}{\partial A}\Delta A\right)\cos(\omega t + \Delta\phi) - \left(2LA\frac{d}{dt}\Delta\phi + A\frac{\partial X_a}{\partial A}\Delta A\right)\sin(\omega t + \Delta\phi) \\ = v_a(t) + v_L(t) \end{aligned}$$

Multiplying by $\cos(\omega t + \Delta\phi)$ or $\sin(\omega t + \Delta\phi)$ and integrating over one period of oscillation, $T = \frac{2\pi}{\omega}$, one has

$$\begin{aligned} 2L\frac{d}{dt}\Delta A - A\frac{\partial R_a}{\partial A}\Delta A &= \frac{\omega}{\pi} \int_{t-\frac{\pi}{\omega}}^{t+\frac{\pi}{\omega}} (v_a(t') + v_L(t')) \cos(\omega t' + \Delta\phi) dt' = v_{ac} + v_{Lc} \\ 2LA\frac{d}{dt}\Delta\phi + A\frac{\partial X_a}{\partial A}\Delta A &= -\frac{\omega}{\pi} \int_{t-\frac{\pi}{\omega}}^{t+\frac{\pi}{\omega}} (v_a(t') + v_L(t')) \sin(\omega t' + \Delta\phi) dt' = -(v_{as} + v_{Ls}) \quad . \end{aligned}$$

Here, $v_{ac}(v_{Lc})$ and $v_{as}(v_{Ls})$ are the cosine and sine components of the internal (external) noise voltages,

$$v_a(t) = v_{ac} \cos(\omega t + \Delta\phi) + v_{as} \sin(\omega t + \Delta\phi)$$

$$v_L(t) = v_{Lc} \cos(\omega t + \Delta\phi) + v_{Ls} \sin(\omega t + \Delta\phi)$$

A resistive saturation parameter s and reactive saturation parameter r are introduced and defined by

$$s \equiv -\frac{A}{R_a(A)} \frac{\partial R_a}{\partial A} \quad ,$$

$$r \equiv \frac{A}{R_a(A)} \frac{\partial X_a}{\partial A} \quad .$$

If one uses $-R_a = \frac{-R_0}{1 + \beta A^2}$ for saturated gain, the resistive saturation parameter is

$$s = \frac{2\beta A^2}{1 + \beta A^2} = \begin{cases} 0 & : \beta A^2 \ll 1 & \text{(just above threshold)} \\ 2 & : \beta A^2 \gg 1 & \text{(far above threshold)} \end{cases}$$

$$2L \frac{d}{dt} \Delta A - A \frac{\partial R_a}{\partial A} \Delta A = \frac{\omega}{\pi} \int_{t-\frac{\pi}{\omega}}^{t+\frac{\pi}{\omega}} (v_a(t') + v_L(t')) \cos(\omega t' + \Delta\phi) dt' = v_{ac} + v_{Lc}$$

$$2LA \frac{d}{dt} \Delta\phi + A \frac{\partial X_a}{\partial A} \Delta A = -\frac{\omega}{\pi} \int_{t-\frac{\pi}{\omega}}^{t+\frac{\pi}{\omega}} (v_a(t') + v_L(t')) \sin(\omega t' + \Delta\phi) dt' = -(v_{as} + v_{Ls}) .$$

→ $\frac{d}{dt} \Delta A + \frac{sR_L}{2L} \Delta A = \frac{1}{2L} (v_{ac} + v_{Lc})$

$$\frac{d}{dt} \Delta\phi + \frac{rR_L}{2LA} \Delta A = -\frac{1}{2LA} (v_{as} + v_{Ls})$$

$$v_a(t) = v_{ac} \cos(\omega t + \Delta\phi) + v_{as} \sin(\omega t + \Delta\phi)$$


$$v_L(t) = v_{Lc} \cos(\omega t + \Delta\phi) + v_{Ls} \sin(\omega t + \Delta\phi)$$

The amplitude noise ΔA ← cosine components of the internal and external noise voltages suppressed with the decay rate $\frac{sR_L}{2L} = \frac{s}{2} \left(\frac{\omega}{Q_e} \right)$

where Q_e is a Q factor due to output coupling loss and $\frac{\omega}{Q_e}$ is the associated photon decay rate. The gain saturation represented by the resistive saturation parameter s operates as a restoring force for the amplitude.

The phase noise $\Delta\phi$ ← sine components of the internal and external noise voltages driven by the amplitude noise via the reactive saturation parameter. no restoring force for the phase.

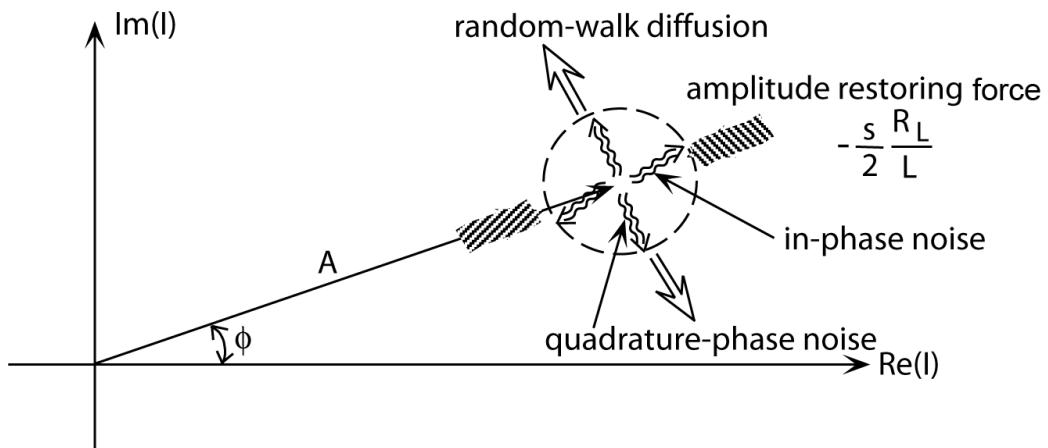the phase of a free-running oscillator diffuses via a random walk, while the amplitude is stabilized to its steady-state value. This effect is shown schematically in Fig. 10.5.



$$\frac{d}{dt} \Delta A + \frac{sR_L}{2L} \Delta A = \frac{1}{2L} (v_{ac} + v_{Lc})$$

$$\frac{d}{dt} \Delta \phi + \frac{rR_L}{2LA} \Delta A = -\frac{1}{2LA} (v_{as} + v_{Ls})$$

F.T. 

$$S_{\Delta A}(\Omega) = \frac{1}{s^2 R_L^2} \cdot \frac{S_{ac}(\Omega) + S_{Lc}(\Omega)}{1 + (\Omega/\Omega_c)^2},$$

$$S_{\Delta \phi}(\Omega) = \frac{\left(\frac{\omega}{Q_e}\right)^2}{4A^2 R_L^2 \Omega^2} [S_{as}(\Omega) + S_{Ls}(\Omega)] + \frac{\left(\frac{r}{s}\right)^2 \left(\frac{\omega}{Q_e}\right)^2}{4A^2 R_L^2 \Omega^2} \cdot \frac{S_{ac}(\Omega) + S_{Lc}(\Omega)}{1 + (\Omega/\Omega_c)^2}.$$

,where the noise bandwidth Ω_c is given by

$$\Omega_c = \frac{s}{2} \left(\frac{\omega}{Q_e} \right) = \begin{cases} 0 & : \beta A^2 \ll 1 \quad (\text{just above threshold}) \\ \frac{\omega}{Q_e} & : \beta A^2 \gg 1 \quad (\text{far above threshold}) \end{cases}$$

At far above threshold, the amplitude noise spectrum is reduced to

$$S_{\Delta A}(\Omega) = \frac{1}{4R_L^2} \cdot \frac{S_{ac}(\Omega) + S_{Lc}(\Omega)}{1 + \left(\Omega/\frac{\omega}{Q_e}\right)^2}$$

Two limiting cases:

(1) Quantum Limit: $S_{ac}(\Omega) = S_{Lc}(\Omega) = 4\hbar\omega R_L$

 $S_{\Delta A}(\Omega) = \frac{\frac{2\hbar\omega}{R_L}}{1 + \left(\Omega/\frac{\omega}{Q_e}\right)^2}$

(2) Thermal Limit: $S_{ac}(\Omega) = S_{Lc}(\Omega) = 8k_B T R_L$

 $S_{\Delta A}(\Omega) = \frac{\frac{4k_B T}{R_L}}{1 + \left(\Omega/\frac{\omega}{Q_e}\right)^2}$


Remember that $\frac{1}{2}LA^2 = \hbar\omega n$, where n = the # of oscillator photons.

$$S_{\Delta n}(\Omega) = \left(\frac{LA}{\hbar\omega}\right)^2 S_{\Delta A}(\Omega) = \begin{cases} 4n \cdot \frac{\left(\frac{\omega}{Q_e}\right)^{-1}}{1 + \left(\Omega/\frac{\omega}{Q_e}\right)^2} & : \text{Quantum limit} \\ 4n \left(\frac{2k_B T}{\hbar\omega}\right) \frac{\left(\frac{\omega}{Q_e}\right)^{-1}}{1 + \left(\Omega/\frac{\omega}{Q_e}\right)^2} & : \text{Thermal limit} \end{cases}$$

Therefore, the variance in the photon number $\langle \Delta n^2 \rangle$ is calculated by the Parseval theorem:

$$\langle \Delta n^2 \rangle \equiv \int_0^\infty S_{\Delta n}(\Omega) \frac{d\Omega}{2\pi} = \begin{cases} n & : \text{Quantum limit} = \text{Poissonian} \\ 2nn_{\text{th}} & : \text{Thermal limit} > \text{Poissonian} \end{cases}$$

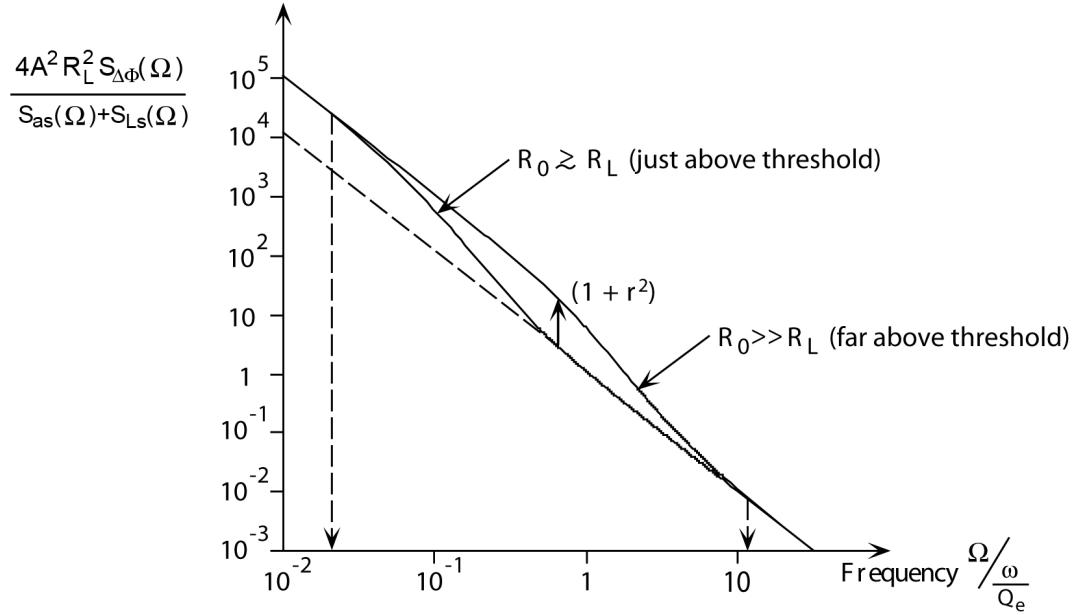The phase noise spectra of a laser oscillator



If we define an instantaneous frequency by

$$\Delta\omega(t) = \frac{d}{dt}\Delta\phi(t) \quad ,$$

the frequency noise spectrum is given by

$$\begin{aligned} S_{\Delta\omega}(\Omega) &= \Omega^2 S_{\Delta\phi}(\Omega) \\ &= \frac{\left(\frac{\omega}{Q_{ex}}\right)^2}{4A^2 R_L^2} [S_{as}(\Omega) + S_{Ls}(\Omega)] + \frac{\left(\frac{r}{s}\right)^2 \left(\frac{\omega}{Q_{ex}}\right)^2}{4A^2 R_L^2} \cdot \frac{[S_{ac}(\Omega) + S_{Lc}(\Omega)]}{1 + (\Omega/\Omega_c)^2} \quad . \end{aligned}$$

The frequency noise enhancement factor

$$\begin{aligned} \frac{r}{s} &\equiv \left(\frac{A}{R_a(A)} \frac{\partial X_a}{\partial A} \right) / \left(-\frac{A}{R_a(A)} \frac{\partial R_a}{\partial A} \right) \\ &= - \left(\frac{\partial X_a}{\partial A} \right) / \left(\frac{\partial R_a}{\partial A} \right) \\ &= - \left(\frac{\partial \chi_r}{\partial A_0} \right) / \cdot \left(\frac{\partial \chi_i}{\partial A_0} \right) \quad . \end{aligned}$$

= a linewidth enhancement factor, Henry's α -parameter

Spectral Linewidth

The oscillator circuit impedance = $Z(\omega) = 2L \left[\frac{1}{2Q} \omega + i(\omega - \omega'_0) \right]$

, where $\omega'_0 = \omega_0 - \frac{X_a(A)}{2L}$ = actual oscillation frequency
 cold cavity resonant frequency

& the effective (or active) Q-value

$$\frac{\omega}{Q} \equiv \frac{\omega}{Q_e} - \frac{\omega}{Q_a} = \frac{R_L}{L} - \frac{R_a(A)}{L}$$


The spectral profile of the oscillating current

$$\overline{|i(\omega)|^2} = \frac{S_{v_a}(\omega'_0) + S_{v_L}(\omega'_0)}{4L^2 \left[\frac{1}{4} \left(\frac{\omega}{Q} \right)^2 + (\omega - \omega'_0)^2 \right]} \quad \begin{array}{l} \text{Lorentzian profile} \\ \text{with FWHM } \Delta\omega_{1/2} = \frac{\omega}{Q} \end{array}$$

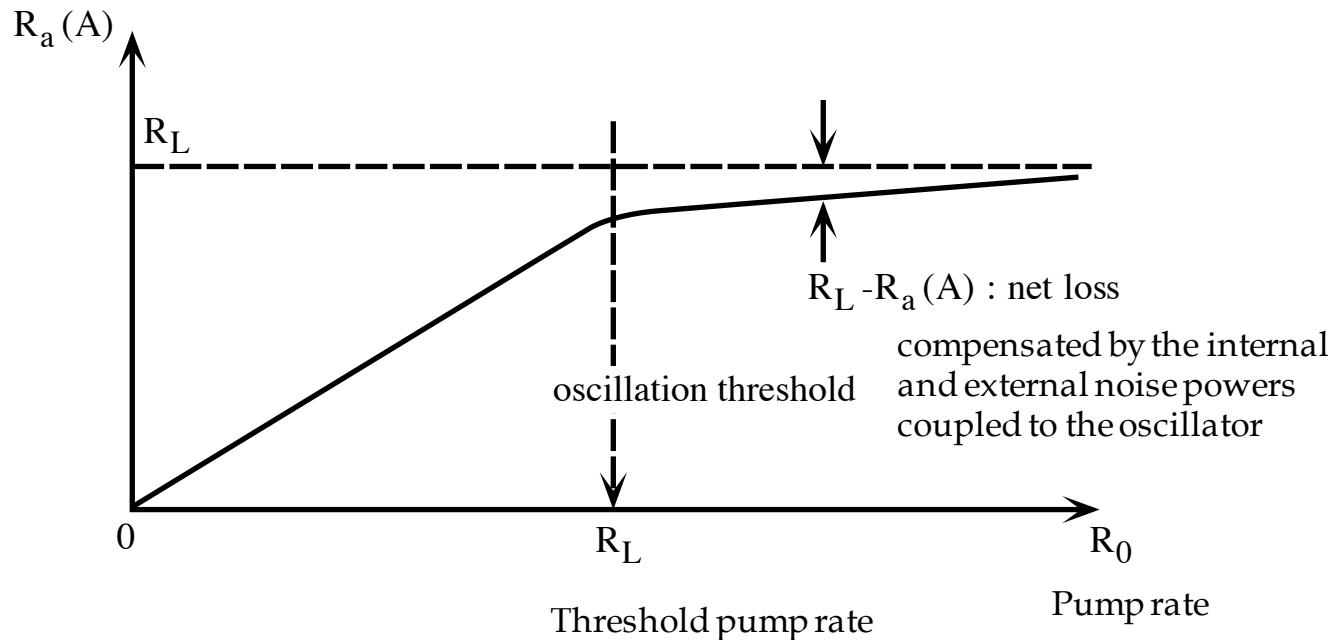(1) Below the Oscillation Threshold

$$\Delta\omega_{1/2} = \frac{\omega}{Q_e} \left(1 - \frac{R_0}{R_L} \right) \leftarrow \begin{array}{l} \text{gain saturation is negligible,} \\ R_a(A) \simeq R_0 \end{array}$$

Decreases linearly with the difference $(R_L - R_0)$



Spectral Linewidth

(2) Above the Oscillation Threshold

Let us first compute the emitted power

$$\begin{aligned} P_e &= R_L \int_0^\infty \overline{|i(\omega'_0)|^2} \frac{d\omega}{2\pi} \\ &= \frac{R_L}{4L^2 \left(\frac{\omega}{Q}\right)} \left[S_{v_a}(\omega'_0) + S_{v_L}(\omega'_0) \right] . \end{aligned}$$

(2-A) Quantum Limit: $S_{v_a}(\omega'_0) = S_{v_L}(\omega'_0) = 2\hbar\omega'_0 R_L$

$$\Delta\omega_{1/2} \equiv \frac{\omega}{Q} = \frac{\hbar\omega'_0 \left(\frac{\omega}{Q_e}\right)^2}{P_e} .$$

If one uses $\Delta\nu_{1/2} = \frac{1}{2\pi} \Delta\omega_{1/2}$ and $\Delta\nu_c = \frac{1}{2\pi} \left(\frac{\omega}{Q_e}\right)$, one obtains

$$\Delta\nu_{1/2} = \frac{2\pi h\nu'_0 (\Delta\nu_c)^2}{P_e} .$$

This is the Schawlow-Townes linewidth for a laser oscillator. |

(2-B) Thermal Limit: $S_{v_a}(\omega'_0) = S_{v_L}(\omega'_0) = 4k_B T R_L$

$$\Delta\omega_{1/2} = \frac{2k_B T \left(\frac{\omega}{Q_e}\right)^2}{P_e} ,$$

$$\Delta\nu_{1/2} = \frac{4\pi k_B T (\Delta\nu_c)^2}{P_e} .$$

This is the Shimoda-Takahashi-Townes linewidth for a maser oscillator.

Spontaneous Emission Coupling Efficiency

Recall $P_{\text{out}} = \hbar\omega A_0^2 \left(\frac{\omega}{Q_e} \right) = \frac{1}{2} R_L A^2$ and $A^2 = \frac{1}{\beta} \left(\frac{R_0}{R_L} - 1 \right)$

, where β = saturation parameter

The spectral linewidth $\Delta\omega_{1/2}$ in the quantum limit $\Delta\omega_{1/2} = \left(\frac{\omega}{Q_e} \right) \frac{2\beta \frac{\hbar\omega_0'}{L}}{\left(\frac{R_0}{R_L} - 1 \right)}$

$2\beta \hbar\omega_0' / L$ = the inverse of the saturation photon number

$$n_s = \frac{L}{2\hbar\omega_0' \beta}$$

The spontaneous emission coupling efficiency is defined as the fractional rate of spontaneous emission coupled into a single laser mode out of the total spontaneous emission rate.

$$\xi = \frac{1}{n_s} = \frac{2\hbar\omega_0' \beta}{L}$$

Laser threshold definition: an average photon number of a laser mode = spontaneous emission rate = stimulated emission rate

$$n = \xi P_{\text{th}} \tau_{\text{ph}} = 1 \longrightarrow P_{\text{th}} = \frac{1}{\xi \tau_{\text{ph}}} = \frac{\left(\frac{\omega}{Q_e} \right)}{\xi}$$


Photon number

$$n = \xi P \tau_{\text{ph}} = \xi \frac{P}{\left(\frac{\omega}{Q_e} \right)}$$

below threshold

$$n = n_s (P/P_{\text{th}} - 1) = \frac{1}{\xi} (P/P_{\text{th}} - 1)$$

above threshold

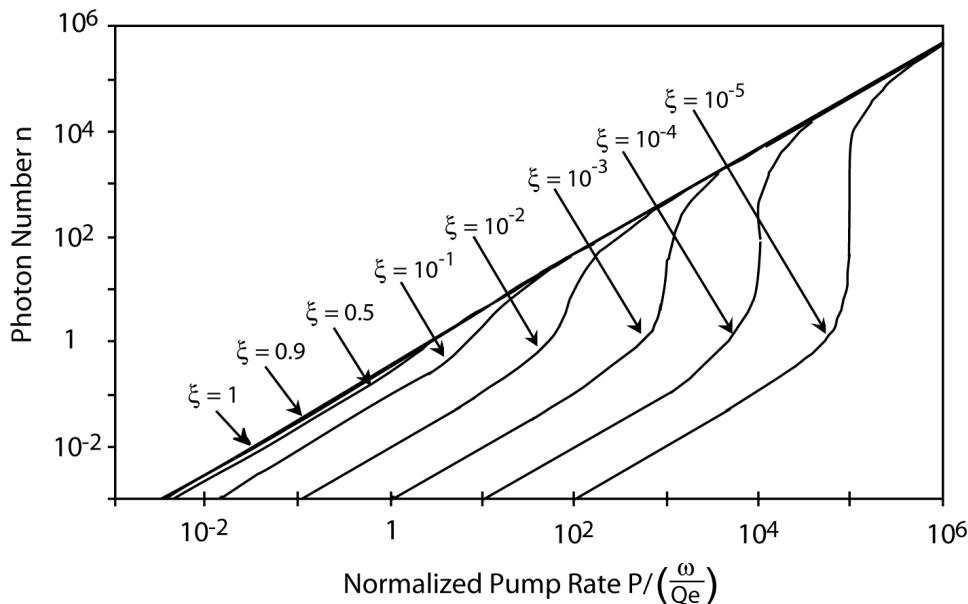


Spectral linewidth

$$\Delta\omega_{1/2} = \frac{\omega}{Q_e} (1 - P/P_{\text{th}})$$

below threshold

$$\Delta\omega_{1/2} = \frac{\left(\frac{\omega}{Q_e}\right)}{n} = \xi \left(\frac{\omega}{Q_e}\right) \frac{1}{P/P_{\text{th}} - 1}$$

above threshold

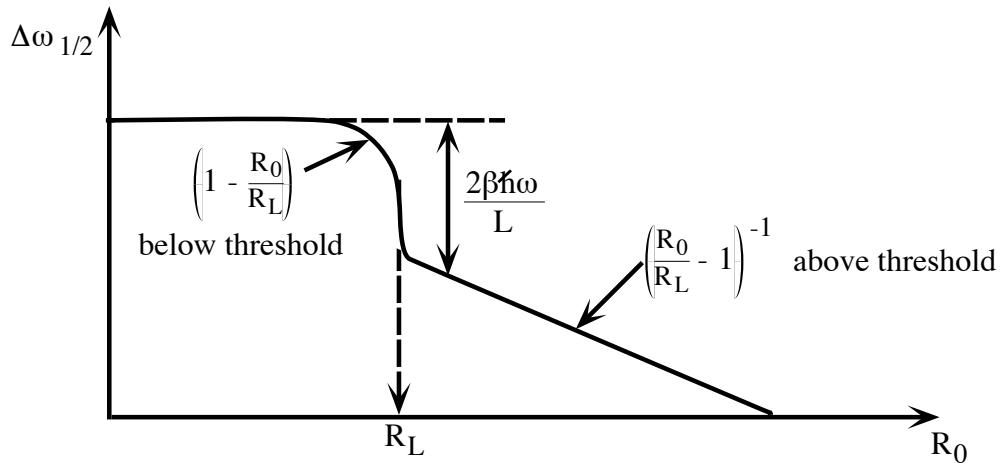

Gain saturation

above threshold : the total spontaneous emission rate is pinned at the threshold power (=gain saturation)

Below threshold : the total spontaneous emission rate is linearly increasing with the power

